

# SOC-Design Lab3 FIR

**github link** (<https://github.com/Charlee0207/SOC-Design/tree/main/Lab3>)

**report link** (<https://hackmd.io/ZRIFy4t8Rai-nfZyGJMa9A?both>)

NTHU EECS24 109020014 李承瀚

## Brief introduction

### Resource Constraints

This lab focuses on implementing a Finite Impulse Response (FIR) engine in Verilog. The FIR design is constrained to have 11 taps, and it must use only one adder and one multiplier.

### Communacation Protocal

To control and monitor the FIR system, the host or testbench initiates the system by signaling the `ap_start` . The system's operational status can be gauged through `ap_idle` and `ap_done` signals, which the host/testbench continuously polls. This communication is established using the AXI-Lite protocol.


Subsequent to the initial communication, the input data `x[n]` is streamed into the system . In response, the output `y[n]` is streamed back to the host. This data transfer is using the AXI-Stream protocol.

Furthermore, both the coefficient `h[n]` and the input data `x[n]` need to be stored in the BRAM.

## Block diagram
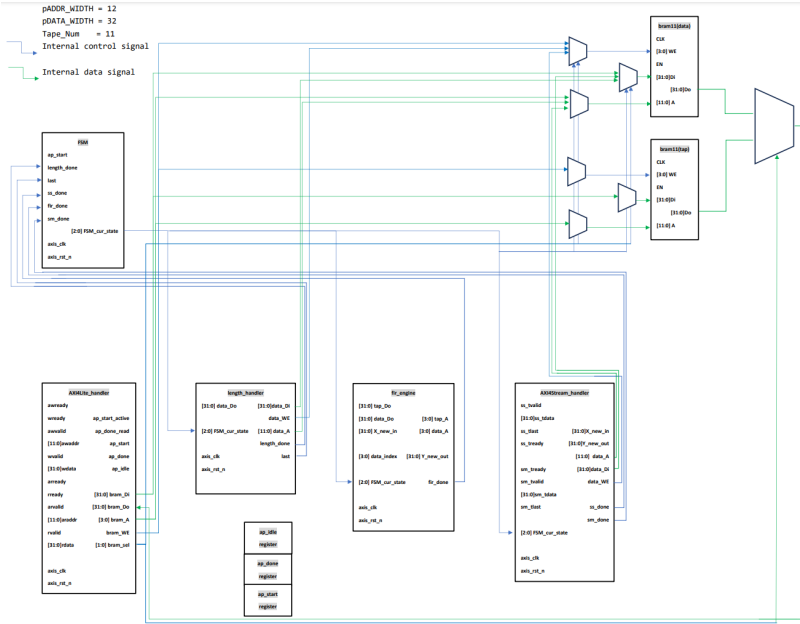
### Datapath

6 modules: FSM , AXI4Lite\_handler , length\_handler , fir\_engine , AXI4Stream\_handler



### Control signals

In FSM , the `[2:0] FSM_cur_state` stores the main control signal, including

`IDLE` , `CHECK_LEN` , `STREAM_IN` , `FIR_COMP` , `DONE` , `STREAM_OUT` .

And the `ap_start` , `length_done` , `last` , `ss_done` , `fir_done` and `sm_done` are asserted by host, `length_handler` , `length_handler` , `AXI4Stream_handler` , `fir_engine` and `AXI4Stream_handler` , respectively.

## Operation description

### FSM phases

#### 1. IDLE Phase

- The FIR system remains in an idle state.
- The host have to program the coefficients, represented by `h[n]` , and also set the data length, `N` , during this phase.

#### 2. CHECK\_LEN Phase

- The `length_handler` is invoked during this phase.

- Its primary function is to decrement the data length value by 1.
- When the data length reach zero, the `length_handler` will raise the `last` signal, signifying the end of data input.

### 3. STREAM\_IN Phase

- The phase signifies the activation of the `AXI4Stream_handler`, initiating the reception of input data denoted by `x`.
- Once the reception process is complete, the `ss_done` signal is asserted to indicate the successful receipt of data.

### 4. FIR\_COMP Phase

- This is the computation phase, where the `fir_engine` takes over.
- It processes the newly received data, the existing data in the shiftRAM, and the tapRAM to generate the desired output.
- Upon successful computation, the `fir_done` signal is asserted.

### 5. STREAM\_OUT Phase

- The `AXI4Stream_handler` is re-invoked, but this time to dispatch the newly computed result `y`, back to the host.
- After successfully transmitting the result to the host, the `sm_done` signal is raised to signify the completion of the transmission.

### 6. DONE Phase

- This phase signifies the completion of the current iteration of computation. The `FSM`, at this juncture, checks for the assertion of the `last` signal.
- Based on the status of this signal, the `FSM` decides its next state - either returning to the `IDLE` phase or proceeding to the `CHECK_LEN` phase.

## Receiving coefficient `h[n]` and `ap_start`

During the `IDLE` phase, the system is configured to accept the coefficient `h[n]` and the signal `ap_start`. The process for this reception and transmission is managed by the `AXI4Lite_handler`.

In scenarios where the handler identifies simultaneous read and write requests, priority is given to the write request.

Its workflow can be summarized as follows:

```

1  /***Handling write address channel**
2  // Check awvalid and write status, and assert wready
3  if(awvalid && !write_flag) begin
4      wready <= 1; wready <= 0; write_flag <= 1; //...other operation
5  end
6  // Deassert wready and assert wready
7  else if(awvalid && wready && write_flag) begin
8      wready <= 0; wready <= 1; write_flag <= 1; //...other operation
9  end
10 /***Handling write data channel**
11 // master hasn't asserted wvalid yet
12 else if(wready && !wvalid && write_flag) begin
13     wready <= 0; wready <= 1; write_flag <= 1; //...other operation
14 end
15 // master assert wvalid, transmit data and deassert wready and write flag
16 else if(wready && wvalid && write_flag) begin
17     wready <= 0; wready <= 0; write_flag <= 0; //...other operation
18 end
19 // Write transaction failed, reset all bit
20 else begin
21     wready <= 0; wready <= 0; write_flag <= 0;
22 end
23
24 //=====
25 /***Handling read address channel in the same way**
26 /***Handling read data channel in the same way**

```

Upon successful reception of data, the next step involves determining where to write this data based on the memory-mapped address.

- **The programming target is `ap_start`**

Since `ap_start` is W/R, `ap_start` cannot be multi-driven by `AXI4Lite_handler` and top module. Hence, it assert `ap_start_active` signal try to

program target. And later when detecting a posedge clk, the `ap_start` controller will update it using value of `ap_start_active`.

- **The programming target is `coefficient`**

It will subtract the `awaddr` by `'h20`, to map to the bram address.

And setup the `bram_sel` to tapRAM, and `bram_WE` to 1.

- **The programming target is `length`**

The length variable is store at `0x00` at dataRAM.

It will setup `bram_A` to `0x00`, `bram_sel` to dataRAM, and `bram_WE` to 1.

### Checking current tap data

As mentioned above, the `AXI4Lite_handler` read request is less prior to write one.

After finishing write request, if `arvalid` is asserted, the handler will connect `bram_A` to corresponding memory position according to `araddr`.

The tap data should be accessable 2 cycles later from bram. So it connects them to `rdata` and ends this transaction.

### Checking current data number

After `ap_start_active` asserted and `ap_start` updated at next posedge clock, the FSM logic changes state to `CHECK_LEN`.

In this stage, the `length_handler` would be invoked to subtract the data length by 1, and assert `length_done` when finishing.

If the data length is 0, which means this is the last iteration, it asserts `last` signal to the system.

### Receiving data `X[n]`

After `length_done` asserted, the FSM logic changes state to `STREAM_IN`.

The `AXI4Stream_handler` receive only 1 data of `x` by asserting `ss_ready` once when `ss_valid` once.

And after that, it asserts `ss_done` to tell FSM change state.

Rather than stored in FF, the new stream-in `x` would be stored to shiftRAM immediately. And it will connect new stream-in `x` outside to `x_new_in`, for `fir_engine` computing the first accumulation.

### Accessing shiftRAM and tapRAM to do computation

In `fir_engine`, we use a `cycle_counter` with case selection to indicate what operation should be done at this point as following.

At `cycle_counter = 0`, we feed the initial bram address.

The bram data is available at `cycle_counter = 2`, and do the computation. After computation, it will assert

`fir_done` when `cycle_counter = 12` and deassert at next cycle.

In this implementaion, we use a 11DW bram, the `0x00` is used to store `length`. To maintain the shift data order, we use `data_index` to indicate the position and update at `CHECK_LEN` state.

```

1 // ... other operation
2 else if(FSM_cur_state==FIR_COMP)begin
3     case(cycle_counter)
4         'd0: begin
5             tap_A <= 0; data_A <= data_index;
6             // ... other operation
7         end
8         'd1: begin
9             tap_A <= tap_A + 1;
10            data_A <= (data_A=='d1) ? 'd10 : data_A-1;
11            // ... other operation
12        end
13        'd2: begin
14            tap_A <= tap_A + 1;
15            data_A <= (data_A=='d1) ? 'd10 : data_A-1;
16            accumulation <= tap_Do * X_new_in;
17            // ... other operation
18        end
19        'd3, 'd4, 'd5, 'd6, 'd7,
20        'd8, 'd9, 'd10,'d11: begin
21            tap_A <= tap_A + 1;
22            data_A <= (data_A=='d1) ? 'd10 : data_A-1;
23            accumulation <= (bram_valid)
24                ? accumulation + tap_Do*data_Do : accumulation;
25            // ... other operation
26        end
27        'd12: begin
28            tap_A <= 0; data_A <= 0;
29            accumulation <= accumulation;
30            // ... other operation
31        end
32        'd13: begin
33            tap_A <= 0; data_A <= 0;
34            accumulation <= accumulation;
35            // ... other operation
36        end
37        default: begin
38            tap_A <= 0; data_A <= 0;
39            accumulation <= accumulation;
40            // ... other operation
41        end
42    endcase
43 end

```

## Transmitting the result Y[n]

After `fir_done` asserted, the FSM logic changes state to `STREAM_OUT` .

The `AXI4Stream_handler` will connect `ss_tdata` to the accumulation FF in `fir_engine` directly.

And just like `STREAM_IN` stage, doing the stream out use similar way.

## FSM next\_state decision

The `next_state` depends on such `<stageName>_done` signals.

```

always@(*)begin
case(FSM_cur_state)
IDLE: begin
    if(ap_start) FSM_next_state = CHECK_LEN;
    else FSM_next_state = FSM_cur_state;
end
CHECK_LEN: begin // update the data length
    if(length_done) FSM_next_state = STREAM_IN;
    else FSM_next_state = FSM_cur_state;
end
STREAM_IN: begin // axis slave receive X data, until ss_done asserted
    if(ss_done) FSM_next_state = FIR_COMP;
    else FSM_next_state = FSM_cur_state;
end
FIR_COMP: begin // fir engine do computation, until fir_done asserted
    if(fir_done) FSM_next_state = STREAM_OUT;
    else FSM_next_state = FSM_cur_state;
end
STREAM_OUT: begin //axis master transmit new result, until sm_done asserted
    if(sm_done) FSM_next_state = DONE;
    else FSM_next_state = FSM_cur_state;
end
DONE: begin // check continue do fir or goto idle
    if(last) FSM_next_state = IDLE;
    else FSM_next_state = CHECK_LEN;
end
default: begin FSM_next_state = FSM_cur_state; end
end

```

## Generation of ap\_done and ap\_idle

- `ap_done`

If the system finishes the last computation and stream-out, assert `ap_done` .

```

always@(posedge axis_clk) begin
    if(!axis_rst_n)
        ap_done <= 0;
    // deassert ap_done when ap_done was read
    else if(ap_done_read)
        ap_done <= 0;
    // assert ap_done when finished process and transection
    else if(FSM_next_state==DONE && last)
        ap_done <= 1;
    else
        ap_done <= ap_done;
end

```

- `ap_idle`

If the `fir_engine` finishes the last computation but not streaming out yet, assert `ap_idle` .

```

always@(posedge axis_clk) begin
    if(!axis_rst_n)
        ap_idle <= 1;
    else if(ap_start)
        ap_idle <= 0;
    // assert ap_idle when fir finished last processing
    else if(FSM_next_state==STREAM_OUT && last)
        ap_idle <= 1;
    else
        ap_idle <= ap_idle;
end

```

Resource usage (FF, LUT, BRAM)

FF	LUT	TAP BRAM(behavior)	DATA BRAM(behavior)	BRAM(physical)
148 (0.14%)	398 (0.75%)	11	11	0(0%)

Timing report

Minimum clock period

Minimum clock period
10.842





Timing on longest path, slack

Timing on longest path	Slack
10.704	0.001

Max Delay Paths	
-----	
Slack (MET) :	0.001ns (required time - arrival time)
Source:	FSM_onehot_genblk1.FSM_cur_state_reg[4]/C (rising edge-triggered cell FDRE clocked by axis_clk
Destination:	genblk1.u_FIR/genblk1.shift_reg[31]/D (rising edge-triggered cell FDRE clocked by axis_clk
Path Group:	axis_clk
Path Type:	Setup (Max at Slow Process Corner)
Requirement:	10.842ns (axis_clk rise@10.842ns - axis_clk rise@0.000
Data Path Delay:	10.704ns (logic 7.856ns (73.390%) route 2.848ns (26.6
Logic Levels:	9 (CARRY4=4 DSP48E1=2 LUT2=2 LUT4=1)
Clock Path Skew:	-0.145ns (DCD - SCD + CPR)
Destination Clock Delay (DCD):	2.128ns = ( 12.970 - 10.842 )
Source Clock Delay (SCD):	2.456ns
Clock Pessimism Removal (CPR):	0.184ns
Clock Uncertainty:	0.035ns ((TSJ^2 + TIJ^2)^1/2 + DJ) / 2 + PE
Total System Jitter (TSJ):	0.071ns
Total Input Jitter (TIJ):	0.000ns
Discrete Jitter (DJ):	0.000ns
Phase Error (PE):	0.000ns



Simulation Waveform

Programming coefficient, and checking
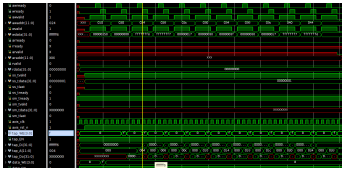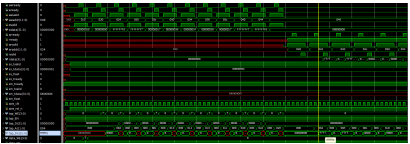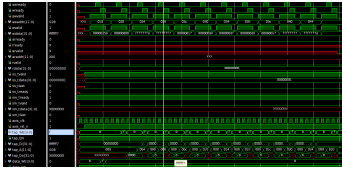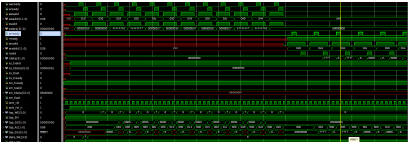
<p>Programming 1st coef.</p> 	<p>Checking 1st coef.</p> 
<p>Programming 2nd coef.</p> 	<p>Checking 2nd coef.</p> 


When `awready` and `awvalid` are sampled, the combinational logic assign the `tap_we` and `tap_di` according to the corresponding `awaddr` . Later, `tap_we` and `tap_di` will be sampled at the rising clock edge, and write data into bram. And the `tap_do` shows the written data after a clock.

Data-in (stream-in)

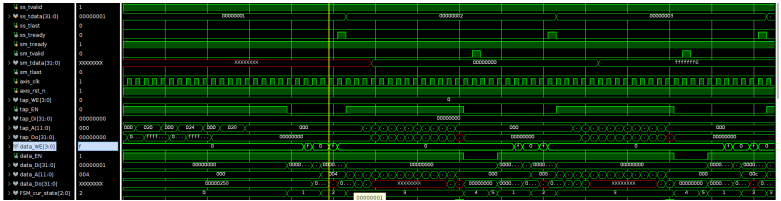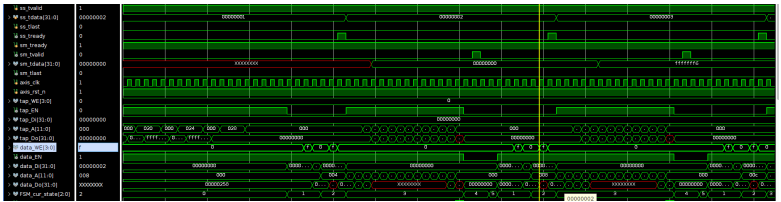
Stream in 1st data	
	
Stream in 2nd data	
	

It first assert `data_we` until the bram transaction finishing. And 1 clock later, it assert `ss_tready` to tell the host to transfer next data.

Data-out (stream-out)

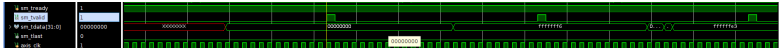Stream out 1st data	
	


### Stream out 2nd data

 


The correct result `sm_tdata` will be sampled by host only when `sm_tvalid`.

## Controlling RAM access


**RAM access of 1st fir**

 


**RAM access of 2nd fir**

 

**RAM access of 3rd fir**

 


RAM access of 4th fir

 


Since we use `bram11` for storing length and shift data, we must maintain the data pointer to read the correct shift data. Which result the first `data_A` address would increase by `0x04`, where the first `tap_A` address is `0x00`, in each iteration of fir computation.

## FSM state transition

### FSM state after ap\_start programmed

 


### FSM state after ap\_start programmed

 

FSM changes the phase correctly when the `done` signal asserted.

## Reason for late submission

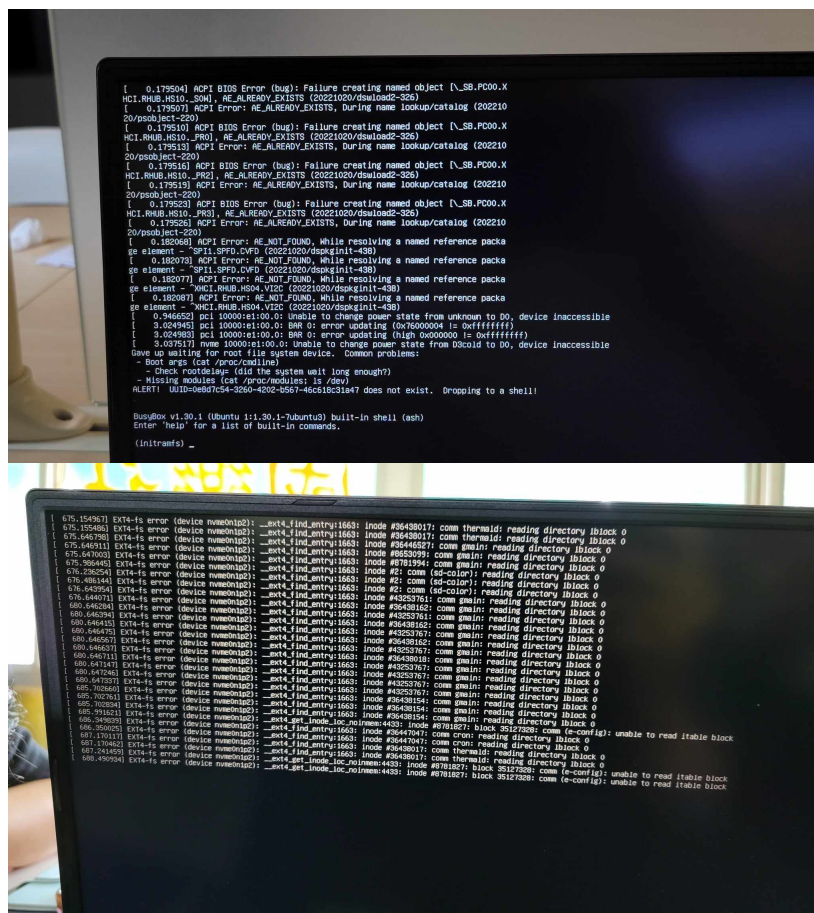

Due to the Notebook SSD failure, I have to use the workstation to do the Lab before the SSD got repaired.